


PhyzJob: Parallel Circuits NUMBER PUZZLES



Apply Ohm's law, Joule's law, and your understanding of the nature of parallel circuits to solve the numerical problems that follow.

Ex. If $\epsilon = 8 \text{ V}$, $R_1 = 12 \Omega$ and $R_2 = 6.0 \Omega$, what is

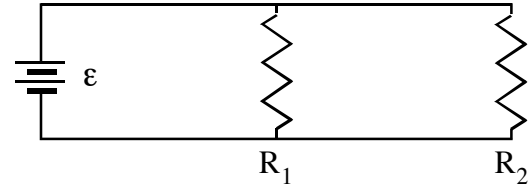- the equivalent resistance of the circuit?
- the total current in the circuit?
- the power dissipated in R_1 ?
- the current through R_2 ?



$$\begin{aligned} \text{a. } R_{\text{EQ}} &= R_1 R_2 / (R_1 + R_2) \\ R_{\text{EQ}} &= 12 \cdot 6 / (12 + 6) \\ R_{\text{EQ}} &= 4 \end{aligned}$$


$$\begin{aligned} \text{b. } I_{\text{TOT}} &= \epsilon / R_{\text{EQ}} \\ I_{\text{TOT}} &= 8 \text{ V} / 4 \\ I_{\text{TOT}} &= 2 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{c. } P_1 &= \epsilon^2 / R_1 \\ P_1 &= (8 \text{ V})^2 / 12 \\ P_1 &= 5.3 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{d. } I_2 &= \epsilon / R_2 \\ I_2 &= 8 \text{ V} / 6 \\ I_2 &= 1.3 \text{ A} \end{aligned}$$

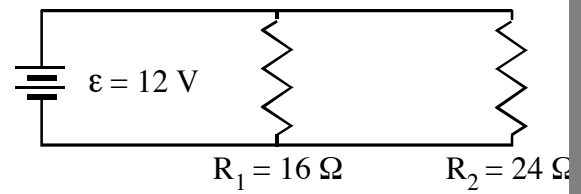1. If $\epsilon = 12 \text{ V}$, $R_1 = 16 \Omega$ and $R_2 = 24 \Omega$, what is

- the equivalent resistance of the circuit?
- the total current in the circuit?
- the power dissipated in R_1 ?
- the current through R_2 ?



$$\begin{aligned} \text{a. } R_{\text{EQ}} &= R_1 R_2 / (R_1 + R_2) \\ R_{\text{EQ}} &= 16 \cdot 24 / (16 + 24) \\ R_{\text{EQ}} &= 9.6 \end{aligned}$$


$$\begin{aligned} \text{b. } I_{\text{TOT}} &= \epsilon / R_{\text{EQ}} \\ I_{\text{TOT}} &= 12 \text{ V} / 9.6 \\ I_{\text{TOT}} &= 1.3 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{c. } P_1 &= \epsilon^2 / R_1 \\ P_1 &= (12 \text{ V})^2 / 16 \\ P_1 &= 9 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{d. } I_2 &= \epsilon / R_2 \\ I_2 &= 12 \text{ V} / 24 \\ I_2 &= 0.5 \text{ A} \end{aligned}$$

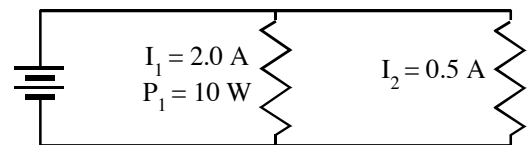2. If $I_1 = 2.0 \text{ A}$, $P_1 = 10 \text{ W}$, and $I_2 = 0.5 \text{ A}$, what is

- the voltage across R_1 ?
- the resistance of R_2 ?
- the power dissipated in the circuit?
- the equivalent resistance of the circuit?



$$\begin{aligned} \text{a. } V_1 &= P_1 / I_1 \\ V_1 &= 10 \text{ W} / 2.0 \text{ A} \\ V_1 &= 5.0 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{b. } R_2 &= \epsilon / I_2 \\ R_2 &= 5.0 \text{ V} / 0.5 \text{ A} \\ R_2 &= 10 \end{aligned}$$

$$\begin{aligned} \text{c. } P_{\text{TOT}} &= I_{\text{TOT}} \epsilon \\ P_{\text{TOT}} &= (2.0 \text{ A} + 0.5 \text{ A}) \cdot 5 \text{ V} \\ P_{\text{TOT}} &= 13 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{d. } R_{\text{EQ}} &= \epsilon / I_{\text{TOT}} \\ R_{\text{EQ}} &= 5 \text{ V} / (2.5 \text{ A}) \\ R_{\text{EQ}} &= 2 \end{aligned}$$

Ω Ω . b W ε I . ε Ω Ω I . d V ε . s . s A ε . 0 . b W ε . ε A ε I . d Ω ε ε . s . I

3. If $I_1 = 1.5 \text{ A}$, $R_1 = 8.0 \ \Omega$, and $R_2 = 6.0 \ \Omega$, what is the voltage across R_2 ?

$$\begin{aligned}V_2 &= V_1 = I_1 R_1 \\V_2 &= 1.5 \text{ A} \cdot 8 \\V_2 &= 12 \text{ V}\end{aligned}$$

4. If $\varepsilon = 9.0 \text{ V}$, $I_1 = 0.4 \text{ A}$, and $I_2 = 1.2 \text{ A}$, what is the power dissipated in the circuit?

$$\begin{aligned}P_{\text{TOT}} &= I_{\text{TOT}} \varepsilon \\P_{\text{TOT}} &= (0.4 \text{ A} + 1.2 \text{ A}) \cdot 9 \text{ V} \\P_{\text{TOT}} &= 14 \text{ W}\end{aligned}$$

5. If $\varepsilon = 32 \text{ V}$, $R_1 = 18 \ \Omega$, and $P_2 = 48 \text{ W}$, what is the current

a. through R_1 ?

b. through R_2 ?

c. through the battery (total current in the circuit)?

$$\text{a. } I_1 = \varepsilon / R_1 = 32 \text{ V} / 18 = 1.8 \text{ A}$$

$$\text{b. } I_2 = P_2 / \varepsilon = 48 \text{ W} / 32 \text{ V} = 1.5 \text{ A}$$

$$\text{c. } I_{\text{TOT}} = I_1 + I_2 = 1.8 \text{ A} + 1.5 \text{ A} = 3.3 \text{ A}$$