


PhyzJob: Series Circuits NUMBER PUZZLES



Apply Ohm's law, Joule's law, and your understanding of the nature of series circuits to solve the numerical problems that follow.

Ex. If $\epsilon = 12\text{ V}$, $R_1 = 3.0\ \Omega$ and $R_2 = 6.0\ \Omega$, what is

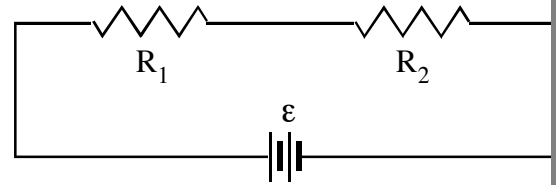- the equivalent resistance of the circuit?
- the total current in the circuit?
- the power dissipated in R_1 ?
- the voltage across R_2 ?



a. $R_{EQ} = R_1 + R_2$ (for series circuit)
 $R_{EQ} = 3.0 + 6.0$
 $R_{EQ} = 9.0$


b. $I = \epsilon / R_{EQ}$
 $I = 12\text{ V} / 9.0$
 $I = 1.3\text{ A}$

c. $P_1 = I^2 R_1$
 $P_1 = (1.3\text{ A})^2 \cdot 3.0$
 $P_1 = 5.1\text{ W}$

d. $V_2 = IR_2$
 $V_2 = 1.3\text{ A} \cdot 6.0$
 $V_2 = 8.0\text{ V}$

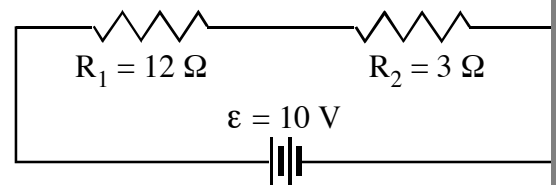1. If $\epsilon = 10\text{ V}$, $R_1 = 12\ \Omega$ and $R_2 = 3.0\ \Omega$, what is

- the equivalent resistance of the circuit?
- the total current in the circuit?
- the power dissipated in R_1 ?
- the voltage across R_2 ?



a. $R_{EQ} = R_1 + R_2$ (for series circuit)
 $R_{EQ} = 12 + 3.0$
 $R_{EQ} = 15$


b. $I = \epsilon / R_{EQ}$
 $I = 10\text{ V} / 15$
 $I = 0.67\text{ A}$

c. $P_1 = I^2 R_1$
 $P_1 = (0.67\text{ A})^2 \cdot 12$
 $P_1 = 5.4\text{ W}$

d. $V_2 = IR_2$
 $V_2 = 0.67\text{ A} \cdot 3$
 $V_2 = 2.0\text{ V}$

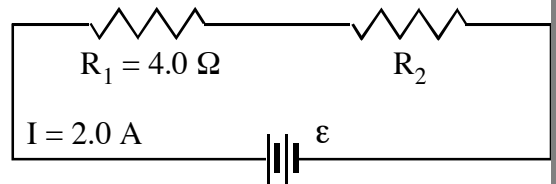2. If $I = 2.0\text{ A}$, $R_1 = 4.0\ \Omega$, and $V_2 = 5.0\text{ V}$, what is

- the voltage across R_1 ?
- the resistance of R_2 ?
- the power dissipated in the circuit?
- the voltage of the battery?



a. $V_1 = IR_1$
 $V_1 = 2.0\text{ A} \cdot 4.0\text{ A}$
 $V_1 = 8.0\text{ V}$

b. $R_2 = V_2 / I$
 $R_2 = 5.0\text{ V} / 2.0\text{ A}$
 $R_2 = 2.5$

c. $P_{TOT} = I^2 R_{EQ}$
 $P_{TOT} = (2.0\text{ A})^2 (4 + 2.5)$
 $P_{TOT} = 26\text{ W}$

d. $\epsilon = IR_{EQ}$
 $\epsilon = 2.0\text{ A} \cdot (4 + 2.5)$
 $\epsilon = 13\text{ V}$

V E I . b W a S . a O m S . d V 0 . 8 . S V 0 . S . b W a S . a A T a . 0 . d O m I . S . I

3. If $\varepsilon = 24 \text{ V}$, $R_1 = 8.0 \ \Omega$, and $R_2 = 6.0 \ \Omega$, what is the current through R_2 ?

$$I = \varepsilon / R_{\text{EQ}}$$
$$I = 24 \text{ V} / (8 + 6)$$
$$I = 1.7 \text{ A}$$

4. If $\varepsilon = 9.0 \text{ V}$, $R_1 = 5.0 \ \Omega$, and $R_2 = 13 \ \Omega$, what is the power dissipated in the circuit?

$$P_{\text{TOT}} = \varepsilon^2 / R_{\text{EQ}}$$
$$P_{\text{TOT}} = (9 \text{ V})^2 / (5 + 13)$$
$$P_{\text{TOT}} = 4.5 \text{ W}$$

5. If $I = 0.75 \text{ A}$, $R_1 = 6 \ \Omega$, and $R_2 = 15 \ \Omega$, what is the voltage

- across R_1 ?
- across R_2 ?
- of the battery?

$$\text{a. } V_1 = IR_1 = 0.75 \text{ A} \cdot 6 = 4.5 \text{ V}$$

$$\text{b. } V_2 = IR_2 = 0.75 \text{ A} \cdot 15 = 11.3 \text{ V}$$

$$\text{c. } \varepsilon = V_1 + V_2 = 4.5 \text{ V} + 11.3 \text{ V} = 15.8 \text{ V}$$