

# PhyzLab: Current Events V

a quantitative investigation of  
compound circuits


PERIOD	1.		
	2.		
GROUP	3.		
	4.		

## • Purpose •

In this activity, you will measure current and voltage at various points in a compound circuit to see how the flow of charge and the energy of that charge are distributed in the circuit.

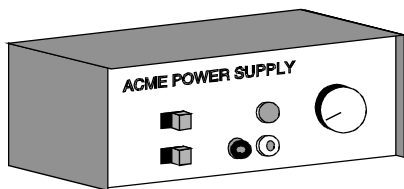
## • Apparatus •

- \_\_\_ variable DC power supply (or 6 V lantern battery)
- \_\_\_ 3 miniature light bulbs in sockets (6.3 V) [#46]
- \_\_\_ 9 connecting wires
- \_\_\_ DC ammeter (0-1 A range)
- \_\_\_ DC voltmeter (0-10 V range) with test leads



*DC power supply*

*NOTE: black terminal is negative*

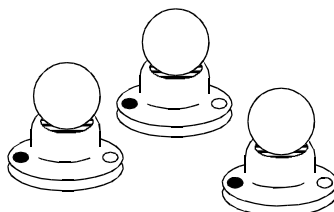



*bulbs in sockets*



*connecting wires*

**THE TEST LEADS ARE ALWAYS CONNECTED TO THE VOLTMETER AND ARE NEVER CONNECTED TO THE AMMETER**


*voltmeter  
(with test leads)*

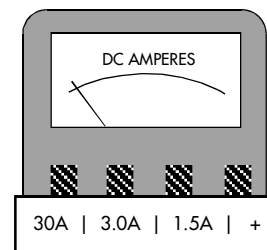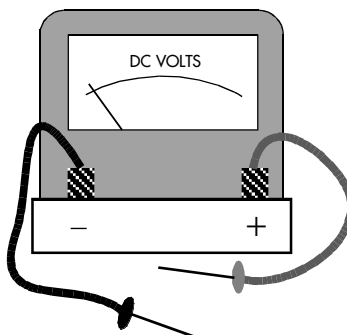


*ammeter*

**1. COMPOUND CIRCUIT A: ONE BULB IN PARALLEL WITH TWO BULBS IN SERIES**

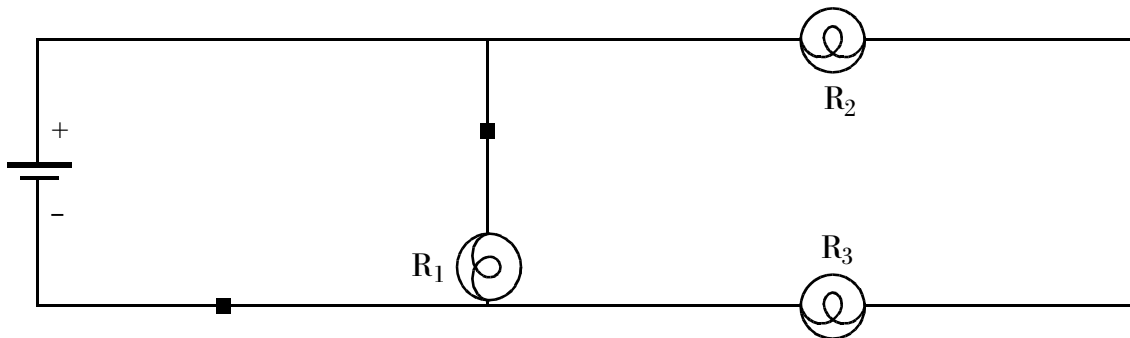a. **Construct** a circuit with three bulbs and **nine** wires as shown below.



SCHEMATIC WITH METERS

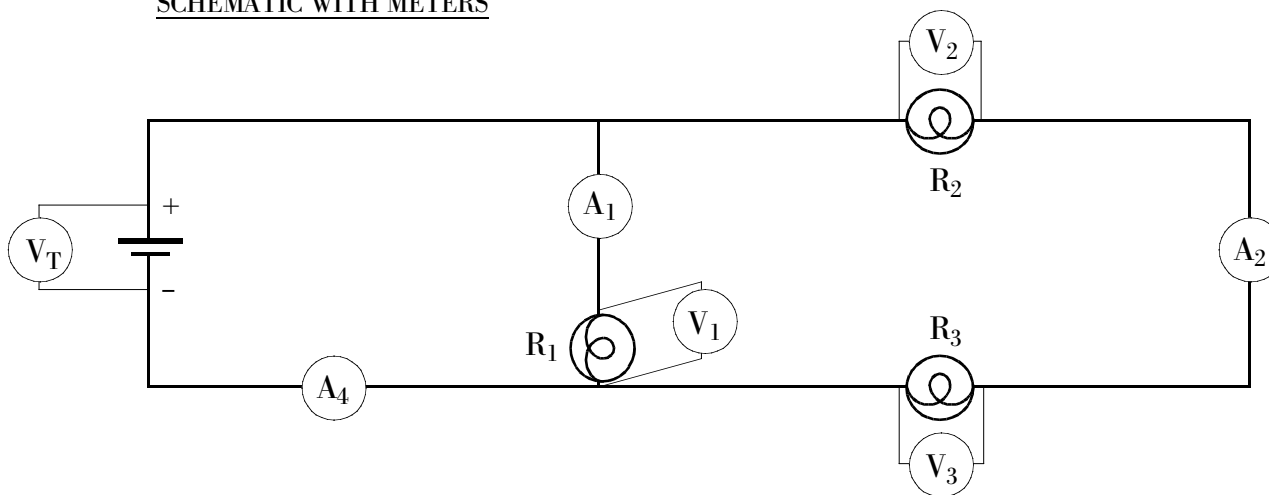

b. **Predict** the values *before* taking measurements (use  $V_T = 6.0\text{ V}$ ):

$V_T = \underline{6.0\text{V}}$

$V_1 = \underline{\hspace{2cm}}$

$I_1 = \underline{\hspace{2cm}}$

$V_2 = \underline{\hspace{2cm}}$

$I_2 = \underline{\hspace{2cm}}$

$V_3 = \underline{\hspace{2cm}}$

$I_3^* = \underline{\hspace{2cm}}$

$I_4 = \underline{0.30\text{ A}}$

c. Set the terminal voltage to 6.0 V and **measure** all quantities listed above and record the values below.

$V_T = \underline{6.0\text{V}}$

$V_1 = \underline{\hspace{2cm}}$

$I_1 = \underline{\hspace{2cm}}$

$V_2 = \underline{\hspace{2cm}}$

$I_2 = \underline{\hspace{2cm}}$

$V_3 = \underline{\hspace{2cm}}$


$I_3^* = \underline{\hspace{2cm}}$

$I_4 = \underline{\hspace{2cm}}$


\* $I_3$  is equal to  $I_2$ ; both are measured by  $A_2$ .

**2. COMPOUND CIRCUIT B: ONE BULB IN SERIES WITH TWO BULBS IN PARALLEL**

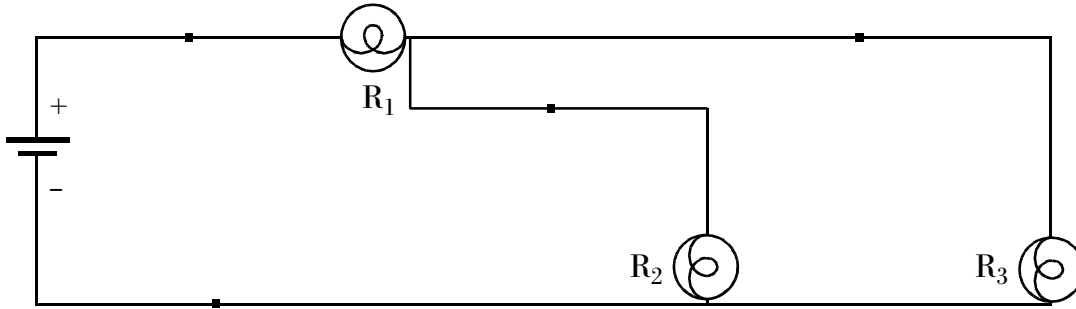a. **Construct** a circuit with three bulbs and **nine** wires as shown below.



SCHEMATIC WITH METERS

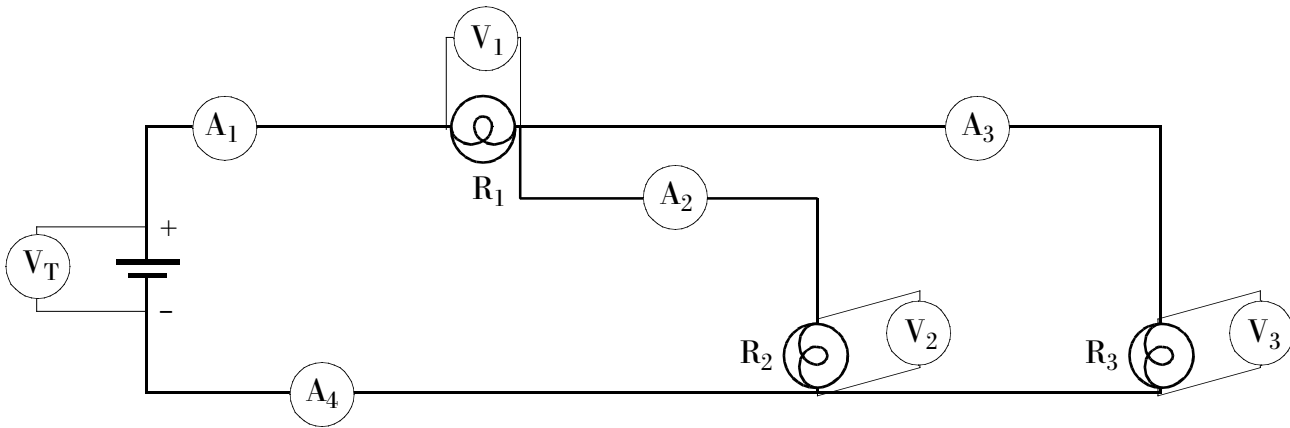

b. **Predict** the values *before* taking measurements (use  $V_T = 6.0V$ ):

$V_T = \underline{6.0V}$

$V_1 = \underline{\hspace{2cm}}$

$I_1 = \underline{0.30 A}$

$V_2 = \underline{\hspace{2cm}}$

$I_2 = \underline{\hspace{2cm}}$

$V_3 = \underline{\hspace{2cm}}$

$I_3 = \underline{\hspace{2cm}}$

$I_4 = \underline{\hspace{2cm}}$

c. Set the terminal voltage to 6.0 V and **measure** all quantities listed above and record the values below.

$V_T = \underline{6.0V}$

$V_1 = \underline{\hspace{2cm}}$

$I_1 = \underline{\hspace{2cm}}$

$V_2 = \underline{\hspace{2cm}}$

$I_2 = \underline{\hspace{2cm}}$

$V_3 = \underline{\hspace{2cm}}$

$I_3 = \underline{\hspace{2cm}}$

$I_4 = \underline{\hspace{2cm}}$

• **Data and Calculations** •

**1. COMPOUND A: ONE BULB IN PARALLEL WITH TWO BULBS IN SERIES.  $V_T =$  \_\_\_\_\_**

	Voltage (V)	Current (A)	Resistance ( )	Power (W)
B <sub>1</sub>				
B <sub>2</sub>				
B <sub>3</sub>				
Tot				

^ Use  $V_T$

^ Use  $I_4$

Power sum ( $P_1 + P_2 + P_3$ ): \_\_\_\_\_

**2. COMPOUND B: ONE BULB IN SERIES WITH TWO BULBS IN PARALLEL.  $V_T =$  \_\_\_\_\_**

	Voltage (V)	Current (A)	Resistance ( )	Power (W)
B <sub>1</sub>				
B <sub>2</sub>				
B <sub>3</sub>				
Tot				

^ Use  $V_T$

^ Use  $I_4$

Power sum ( $P_1 + P_2 + P_3$ ): \_\_\_\_\_

• **Analysis** •

**1. Calculations of Resistance and Power**

Calculate the resistance and power of each bulb and for each circuit in the lab. Record the values in the data table.

**2. Compound Circuit A**

a. In a series circuit, each bulb gets the same current. And the current in each bulb is equal to the total current in the circuit. In a parallel circuit, the current divides among the bulbs; the sum of the currents in the bulbs is equal to the total current in the circuit. What happens to the current in **this** circuit?

b. In a series circuit, the voltage is divided equally among the bulbs; the sum of the voltages across the bulbs is equal to the total voltage provided by the power supply. In a parallel circuit, the voltage across each bulb is the same. And the voltage across each bulb is equal to the terminal voltage of the power supply. What happens to the voltage in **this** circuit?

### 3. Compound Circuit B

a. What happens to the current in **this** circuit?

b. What happens to the voltage in **this** circuit?