
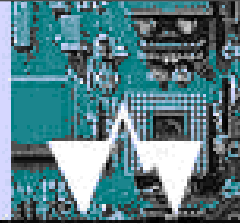


Westwood

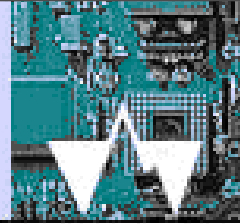


DENVER/HOUSTON/LOS ANGELES/CHICAGO/DENVER/HOUSTON/LOS ANGELES/CHICAGO/DENVER/HOUSTON

Unit 6 Combinatorial Circuits and Boolean Algebras



Combinatorial Circuits and Boolean Algebras

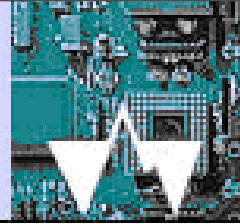- Combinatorial Circuits
- Gates
- AND Gates



Combinatorial Circuits and Boolean Algebras

- OR Gate
- NOT Gate
- Proper subset
- Boolean Expressions
- Properties of Boolean Expressions
- Boolean Algebras